



Daffodil International University

Department of Computer Science and Engineering

Faculty of Science and Information Technology

Final Examination, Semester: Fall - 2019

Course Code: CSE 132

Course Title: Electrical Circuits

Section: All

Course Teacher: All


Time: 2 Hours

Full Marks: 40

Answer all the questions


- 1.a. Determine I , V_1 , V_2 , R_2 for the following circuit.

5

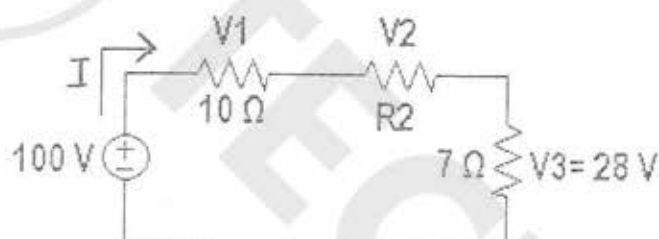


- 1.b. Applying Nodal analysis, find out the node voltages for the following circuit.

5

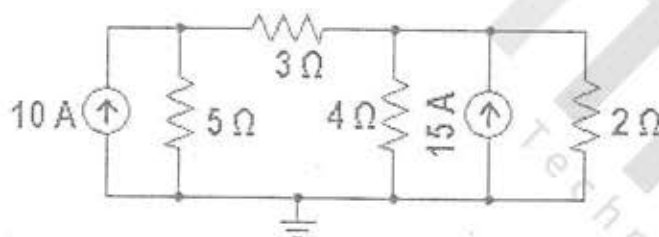

- 2.a. Applying Mesh analysis, determine loop currents for the following circuit.


5

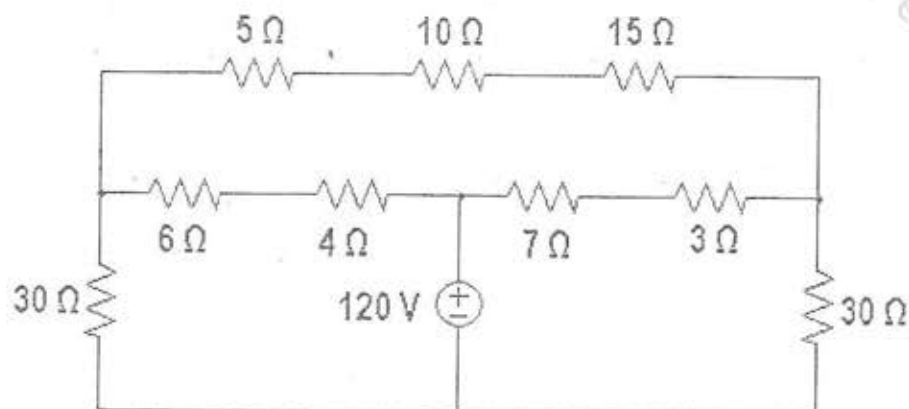

2.b. The current through a $10\text{-}\Omega$ resistor is given, $i = 20 \sin(377t + 45^\circ)$. Find the sinusoidal expression for the voltage. Sketch the v and i curves. 5

3.a. What is power factor? For a pure inductive circuit, determine the phase difference between voltage and current. 5

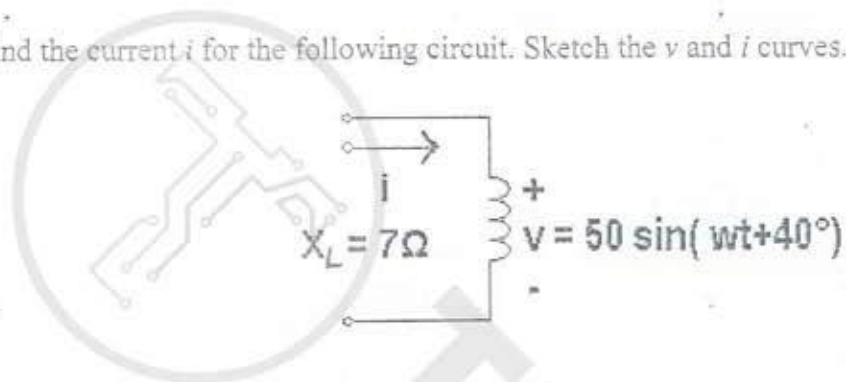3.b. Find the current i for the following circuit. Sketch the v and i curves. 5



4.a. Prove that Average power, $P = V_{rms} I_{rms} \cos\theta$. Also, determine average power for purely resistive, purely inductive and purely capacitive network. 5

4.b. The current through a $120\text{ }\mu\text{F}$ capacitor is given, $i = 70 \sin(500t + 30^\circ)$. Find the sinusoidal expression for the voltage across the capacitor. Also, sketch the v and i curves. 5