



Daffodil International University

Department of Computer Science and Engineering

Faculty of Science and Information Technology

Mid Term Examination, Semester: Fall - 2019

Course Code: CSE 224

Course Title: Electronics Devices and Circuits

Section: All

Course Teacher: All

Time: 1:5 Hrs

Full Marks: 25

Answer any Four out of Five questions (including question no Q5)

- Q1. a. Define forward and reverse biasing of pn junction. 1
b. Describe the properties of semiconductor. 3
c. Can you make crystal diode with n-type Germanium and indium? Describe the alloying method of making pn junction. 3
- Q2. a. We have pulsating dc (pdc), what will be needed to make dc from this pdc? 1
b. Show that the maximum efficiency of a center tap rectifier is double of half wave rectifier. 3
c. Suppose you have ac supply of peak to peak voltage, $V_{pp} = 400$ v and a full wave bridge rectifier, find : (i) I_m , I_{dc} , I_{rms} (ii) ac power input and dc power output of the rectifier (assume internal resistance, $r_f = 1\Omega$ and load resistance $R_L = 998\Omega$). 3
- Q3. a. Find out the relationship between α and β . 1
b. Find the expression of collector current of CE connection of transistor. 3
c. A common base transistor amplifier has an input resistance of 10Ω and output resistance of $100\text{ k}\Omega$. The collector load is $1\text{ k}\Omega$. If a signal of 500 mV is applied between emitter and base, find the voltage amplification. Assume α to be nearly one. 3
- Q4. a. Which one is better JFET or MOSFET? Why? 1
b. If the supply voltage increase and load resistance decrease, how a Zener diode can stabilize the output voltage. Describe in details. 3
c. Design a voltage stabilizer for varying load using a Zener diode of 8 V . The load current is to vary from 12 to 90 mA . Find the value of series resistance R to maintain a voltage of 8 V across the load. The input voltage is constant at 12V and the minimum Zener current is 10 mA . 3
- Q5. a. When pentavalent impurity is added to a pure semiconductor, it is known as and when trivalent impurity is added, it is called semiconductor. 4x1=4
b. The Peak Inverse Voltage of full wave bridge and center tap rectifiers are and respectively.
c. The practical values of base current amplification factor, β varies from to
d. A bipolar junction transistor (BJT) is a controlled device whereas a field effect transistor (FET) is a controlled device.