



Daffodil International University

Department of Computer Science and Engineering

Faculty of Science and Information Technology

Mid Term Examination, Semester: Fall - 2019

Course Code: CSE 132

Course Title: Electrical Circuits

Section: All

Course Teacher: All

Time: 1.5 Hours

Full Marks: 25

Answer all the questions

Q1. State and explain Kirchhoff's voltage law (KVL). 5

Q2. Calculate the equivalent resistance R_{eq} for the circuit of figure 1. 5

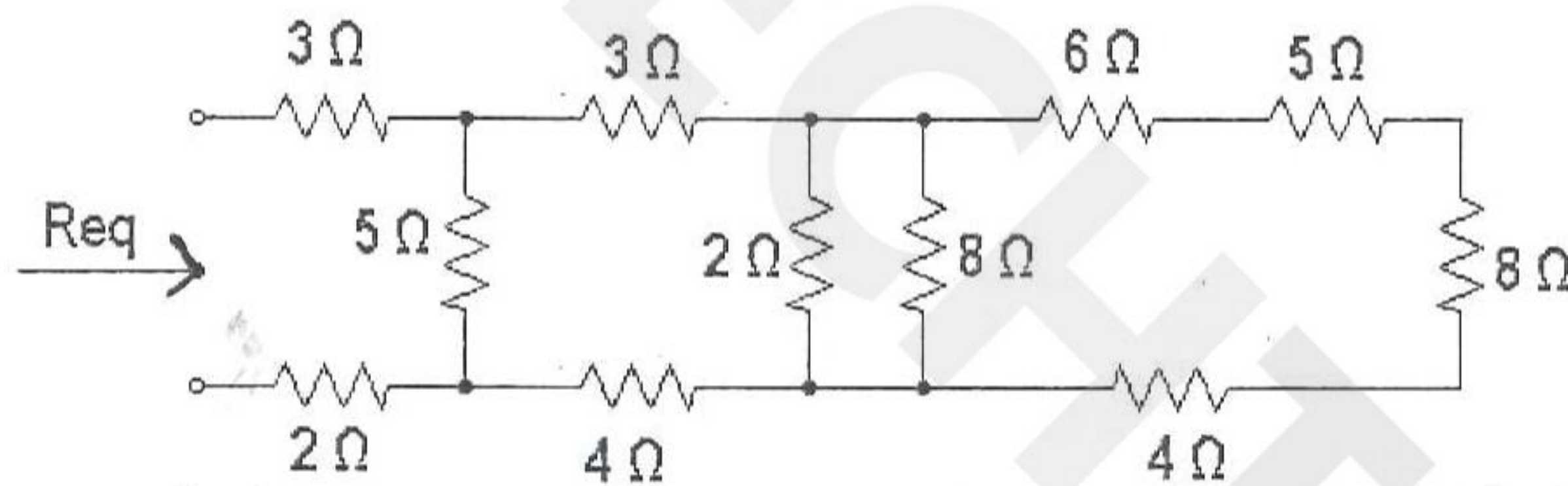


Figure 1

Q3. Determine Current I , i_1 , i_2 , i_3 , i_4 for the circuit of figure 2. 5

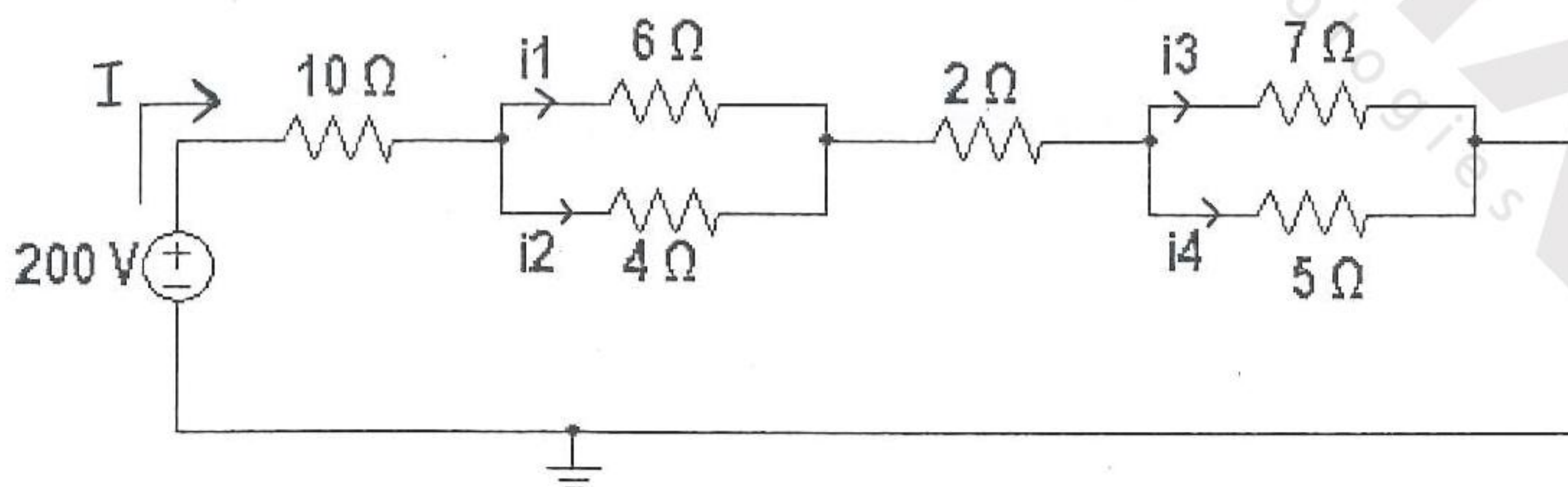


Figure 2

Q4. Using nodal analysis, find out the node voltages for the circuit of figure 3.

5

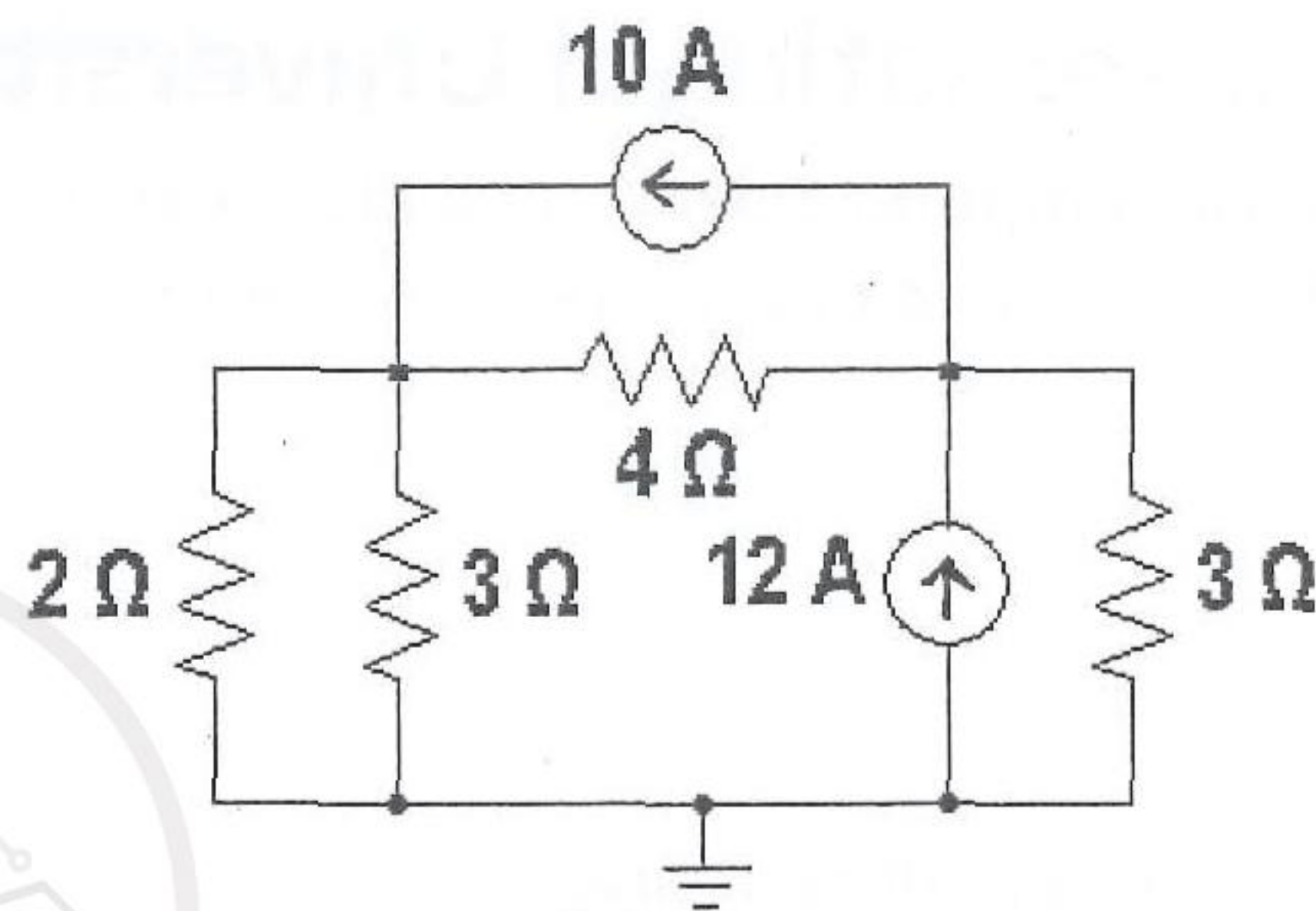


Figure 3

Q5. Using Mesh analysis, determine loop currents for the circuit of figure 4.

5

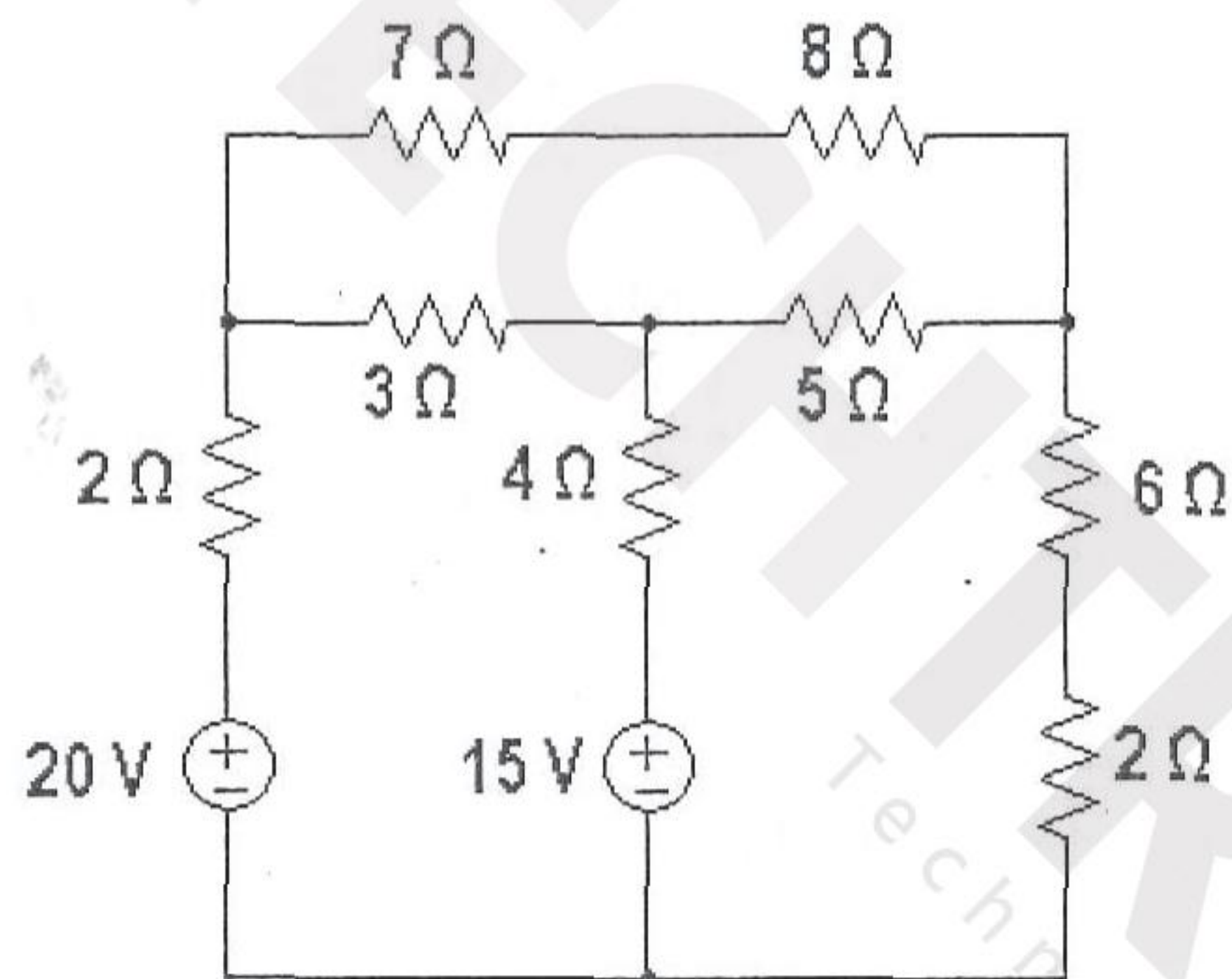


Figure 4